

# *Timing Issues in Multi-level Logic Optimization*

**Giovanni De Micheli**  
***Integrated Systems Centre***  
***EPF Lausanne***



---

This presentation can be used for non-commercial purposes as long as this note and the copyright footers are not removed

© Giovanni De Micheli – All rights reserved

# Module 1

---

## ◆ Objectives:

- ▲ Timing verification:
- ▲ Delay modeling
- ▲ Critical paths
- ▲ The false path problem

# Timing verification and optimization

---

## ◆ Verification:

### ▲ Check that a circuit runs at speed

- ▼ Satisfies I/O delay constraints
- ▼ Satisfies cycle-time constraints

## ◆ Optimization:

### ▲ Minimum *delay*

- ▼ ( subject to *area* constraints )

### ▲ Minimum *area*

- ▼ Subject to *delay* constraints

# Delay modeling

---

- ◆ **Gate delay modeling:**
  - ▲ Straightforward for bound networks
  - ▲ Approximations for unbound networks
- ◆ **Network delay modeling:**
  - ▲ Compute signal propagation
    - ▼ Topological methods
    - ▼ Logic/topological methods (false paths)

# Gate delay modeling unbound networks

---


- ◆ **Virtual gates:**
  - ▲ Logical expressions
- ◆ **Stage delay model:**
  - ▲ Unit delay per vertex
- ◆ **Refined models:**
  - ▲ Depending on fanout

# Network delay modeling

---

- ◆ For each vertex  $v_i$
- ◆ Propagation delay  $d_i$  :
  - ▲ I/O propagation delays are usually zero
- ◆ *Data-ready time*  $t_i$  :
  - ▲ Input data-ready time denote when inputs are available
  - ▲ Computed elsewhere by *forward traversal*
  - ▲  $t_i = d_i + \max_j t_j \quad \text{s.t. } (v_j, v_i) \in E$

# Example

 

## ◆ Propagation delays:

▲  $d_g = 3; d_h = 8; d_m = 1; d_k = 10; d_l = 3$

▲  $d_n = 5; d_p = 2; d_o = 2; d_x = 2; d_y = 3$


# Network delay modeling

---

- ◆ For each vertex  $v_i$  :
- ◆ Required *data-ready time*  $\underline{t}_i$  :
  - ▲ Specified at the primary outputs
  - ▲ Computed elsewhere by *backward traversal*
  - ▲  $\underline{t}_i = \min_j \underline{t}_j - d_j \text{ s.t. } (v_i, v_j) \in E$
- ◆ Slack  $s_i$  :
  - ▲ Difference between required and actual data-ready times
  - $s_i = \underline{t}_j - t_i$



# Example

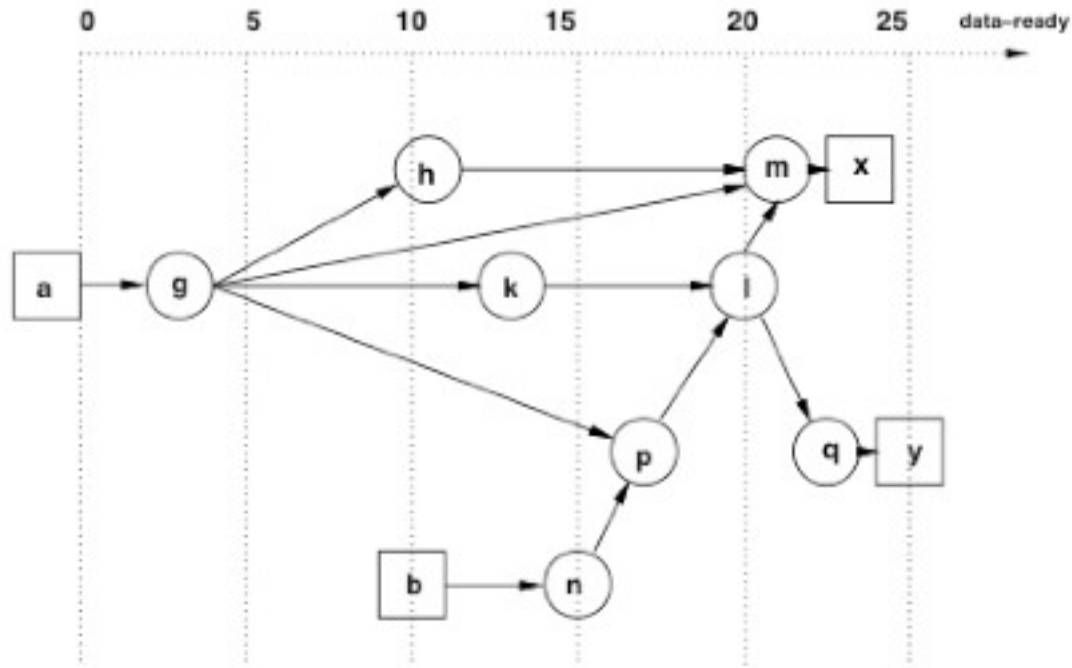


## ◆ Required data-ready times:


▲  $\underline{t}_x = 25$  and  $\underline{t}_y = 25$
 
# Example

- ◆  $s_x = 2; s_y = 0$
- ◆  $t_m = 25 - 2 = 23; s_m = 23 - 21 = 2$
- ◆  $t_q = 25 - 2 = 22; s_q = 22 - 22 = 0$
- ◆  $t_l = \min \{23 - 1; 22 - 2\} = 20; s_l = 20 - 20 = 0$
- ◆  $t_b = 23 - 1 = 22; s_h = 22 - 11 = 11$
- ◆  $t_k = 20 - 3 = 17; s_k = 17 - 13 = 4$
- ◆  $t_p = 20 - 3 = 17; s_p = 17 - 17 = 0$
- ◆  $t_n = 17 - 2 = 15; s_n = 15 - 15 = 0$
- ◆  $t_b = 15 - 5 = 10; s_b = 10 - 10 = 0$
- ◆  $t_g = \min \{22 - 11; 17 - 10; 17 - 2\} = 7; s_g = 7 - 3 = 4$
- ◆  $t_a = 7 - 3 = 4; s_a = 4 - 0 = 4$



# Example

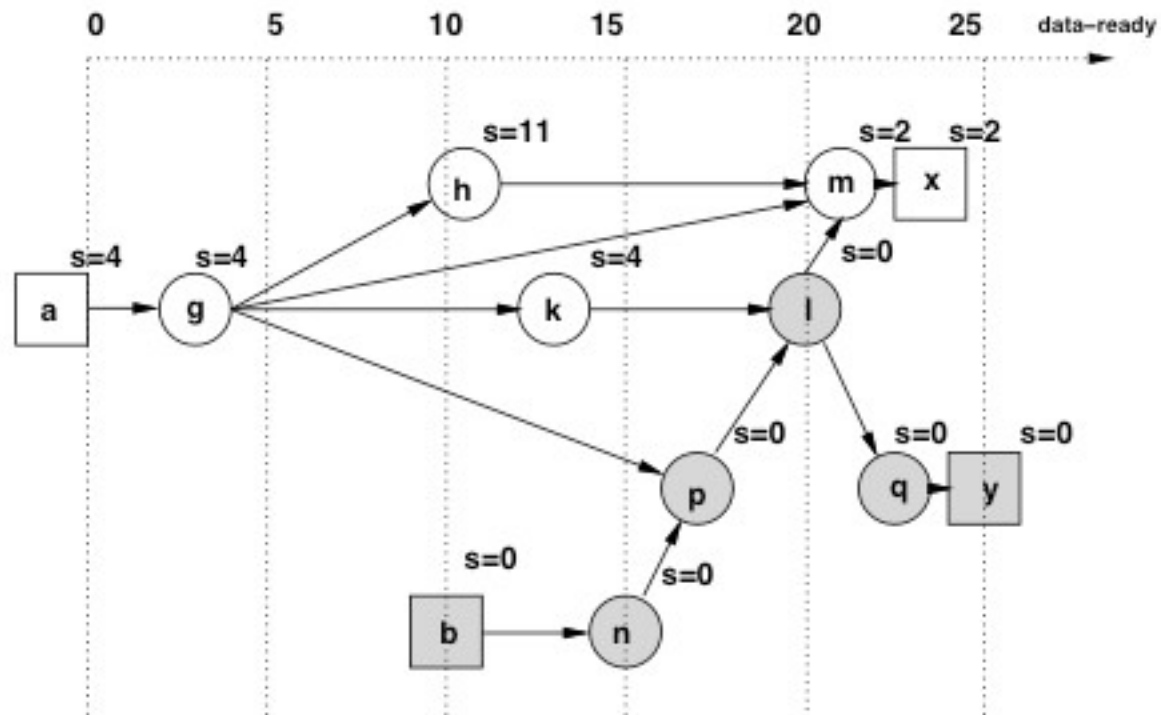


# Topological critical path

---

- ◆ Assume topologic computation of :
  - ▲ Data-ready by forward traversal
  - ▲ Required data-ready by backward traversal
- ◆ *Topological critical path* :
  - ▲ Input/output path with zero slacks
  - ▲ Any increase in the vertex propagation delay affects the output data-ready time
- ◆ A topological critical path may be *false*:
  - ▲ No event can propagate along that path

# Example

 

- ◆ All gates have unit delay
- ◆ All inputs ready at time 0
- ◆ Longest topological path :  $(V_a, V_c, V_d, V_y, V_z)$  :
  - ▲ Path delay: 4 units
- ◆ Critical true path:  $(V_a, V_c, V_d, V_y)$  :
  - ▲ Path delay: 3 units

# Sensitizable paths

---

- ◆ A path in a logic network is *sensitizable* if an event can propagate from its tail to its head
- ◆ A critical *path* is a sensitizable path of maximum weight
- ◆ Only sensitizable paths should be considered
- ◆ Non-sensitizable paths are *false* and can be discarded

# Sensitizable paths

---

- ◆ **Path:**
  - ▲ Ordered set of vertices
- ◆ **Inputs to a vertex:**
  - ▲ Direct predecessors
- ◆ **Side-inputs of a vertex:**
  - ▲ Inputs not on the path

# Dynamic sensitization condition

---

◆ Path:  $P = (v_{xo}, v_{x1}, \dots, v_{xm})$

◆ An event propagates along  $P$  if :


$$\partial f_{xi} / \partial x_{i-1} = 1, i = 1, 2, \dots, m$$

◆ Remarks :

- ▲ Boolean differences are function of the side-inputs and values on the side-inputs may change
- ▲ Boolean differences must be true *at the time that the event propagates*



# Example

 

- ◆ Path:  $(V_a, V_c, V_d, V_y, V_z)$ 
  - ▲  $\partial f_y / \partial d = e = 1$  at time 2
  - ▲  $\partial f_x / \partial y = e' = 1$  at time 3
- ◆ Not dynamically sensitizable because **e** settles at time 1

# Static sensitization


---

- ◆ Simpler, weaker model
- ◆ We neglect the requirement on *when* the Boolean differences must be true to propagate an event
- ◆ There is an assignment of primary inputs **c** such that:

$$\partial f_{x_i}(\mathbf{c}) / \partial x_{i-1} = 1 \quad i=1,2, \dots, m$$

- ◆ May lead to *underestimate* delays

# Example

 

- ◆ Not statically sensitizable

# Example

◆ All gates have unit delay

◆ Topological critical paths:

▲  $\{(v_a, v_d, v_g, v_o); (v_b, v_d, v_g, v_o)\}$

▲ Path delay : 3

▲ Not statically sensitizable

◆ Other path:


▲  $(v_a, v_e, v_o)$

▲ Path delay: 2

◆ Assume:

▲  $c = 0$  and  $a, b$  dropping from 1 to 0

▲ Event propagates to output !!!

 

# Modes for delay computation

---

## ◆ Transition *mode*:

- ▲ Variables assumed to hold previous values
  - ▼ Model circuit node capacitances
- ▲ *Two test vectors* are needed

## ◆ Floating *mode*:

- ▲ Circuit is assumed to be memoryless
  - ▼ Variables have unknown value until set by input test vector
- ▲ Need *only one* test vector

# Modes for delay computation

---




- ◆ *Floating mode* delay computation is simpler than *transition mode* computation
- ◆ *Floating mode* is a pessimistic approach
- ◆ *Floating mode* is more robust:
  - ▲ *Transition mode* may not have the *monotone speed-up* property

# Monotone speed-up property

---

- ◆ Propagation delays are upper bounds:
  - ▲ What happens if gates are *faster* than expected?
- ◆ We must insure that speeding-up a gate does not slow-down the circuit:
  - ▲ Topological critical paths are robust
  - ▲ What about dynamically sensitizable paths in transition mode?

# Example

   

- ◆ Propagation delay: 2 units
- ◆ Shaded gate: 3 units and 1 unit



# Static co-sensitization

---

- ◆ Assumption:
  - ▲ Circuit modeled by *AND*, *OR*, *INV* gates
  - ▲ *INV* are irrelevant to the analysis
  - ▲ Floating mode
- ◆ Controlling values:
  - ▲ 0 for *AND* gate
  - ▲ 1 for *OR* gate
- ◆ Gate has *controlled value*

# Static co-sensitization

---


- ◆ Path:  $P = (v_{xo}, v_{x1}, \dots, v_{xm})$
- ◆ A vector *statically co-sensitizes* a path to 1 (or to 0) if :
  - ▲  $x_m = 1$  (or 0) and
  - ▲  $v_{xi-1}$  has a controlling value whenever  $v_{xi}$  has a controlled value
- ◆ Necessary condition for a path to be true

# False path detection test

---

- ◆ For all input vectors, one of the following is true:
  - ▲ (1) A gate is controlled and
    - ▼ the path provides a non-controlling value
    - ▼ a side-input provides a controlling value
  - ▲ (2) A gate is controlled and
    - ▼ The path and a side-input have controlling values
    - ▼ The side-input presents the controlling value first
  - ▲ (3) A gate is not controlled and
    - ▼ A side-input presents the non-controlling value last

# Example

 

◆ Path:  $(v_a, v_c, v_d, v_y, v_z)$

◆ For  $a = 0, b = 0$  :

▲ Condition (1) occurs at the OR gate

◆ For  $a = 0, b = 1$  :

▲ Condition (2) occurs at the AND gate

◆ For  $a = 1, b = 0$  :

▲ Condition (2) occurs at the OR gate

◆ For  $a = 1, b = 1$  :

▲ Condition (1) occurs at the AND gate

# Important problems

---

- ◆ Check if circuit works at speed  $\underline{t}$  :
  - ▲ Verify that all true paths are faster than  $\underline{t}$
  - ▲ Show that all paths slower than  $\underline{t}$  are false
- ◆ Compute groups of false paths
- ◆ Compute critical true path:
  - ▲ Binary search for values of  $\underline{t}$
  - ▲ Show that all paths slower than  $\underline{t}$  are false

# Module 2

---

## ◆ Objectives:

- ▲ Algorithms for timing optimization
- ▲ Favorable logic transformations

# Algorithms for delay minimization

---

- ◆ Alternate:
  - ▲ Critical path computation
  - ▲ Logic transformation on critical vertices
- ◆ Consider *quasi critical paths*:
  - ▲ Paths with near-critical delay
  - ▲ Small slacks

# Algorithms for delay minimization

---

◆ REDUCE\_DELAY (  $G_n(V,E)$  ,  $\varepsilon$  ) {

*repeat* {

▲ Compute critical paths and critical delay  $\tau$

▲ Set output required data-ready times to  $\tau$

▲ Compute slacks

▲  $U$  = vertex subset with slack lower than  $\varepsilon$

▲  $W$  = select vertices in  $U$

▲ Apply transformations to vertices  $W$

▲ } *until* (no transformation can reduce  $\tau$  )

}



# Transformation for delay reduction

---

- ◆ Reduce propagation delay
- ◆ Reduce dependencies from critical inputs
- ◆ *Favorable* transformation:
  - ▲ Reduces local data-ready time
  - ▲ Any data-ready time increase at other vertices is bounded by the local slack



# Example

---

- ◆ Unit gate delay
- ◆ Transformation:
  - ▲ Elimination
- ◆ Always favorable
- ◆ Obtain several area/delay trade-off points
  
# Example

- ◆ Iteration 1:  
eliminate  $v_p, v_q$ . (No literal increase)
- ◆ Iteration 2:  
eliminate  $v_u$ . (No literal increase)
- ◆ Iteration 3:  
eliminate  $v_r, v_s, v_t$ . (Literal increase)



# More refined delay models

---


## ◆ Elimination:

- ▲ Reduces one stage
- ▲ Yields more complex and slower gates
- ▲ May slow other paths


## ◆ Substitution:

- ▲ Adds one dependency
- ▲ Loads and slows a gate
- ▲ May slow other paths


# Example

 


(a)

 

(b)

 

(c)

 

(d)




# Speed-up algorithm

---

- ◆ Determine a subnetwork  $W$  of depth  $d$
- ◆ Collapse subnetwork by elimination
- ◆ Duplicate vertices with successors outside  $W$ :
  - ▲ Record *area penalty*
- ◆ Resynthesize  $W$  by timing-driven decomposition
- ◆ Heuristics:
  - ▲ Choice of  $W$
  - ▲ Monitor *area penalty* and *potential speed-up*
   
# Example

- ◆ NAND delay = 2  
INV delay = 1
- ◆ All input data-ready are 0, except =  $t_d = 3$



# Minimal-area synthesis under delay constraints

---

- ◆ Start from timing-feasible network
- ◆ *Minimize area* while preserving timing feasibility:
  - ▲ Use area optimization algorithms
  - ▲ Monitor delays and slacks
  - ▲ Reject transformations yielding negative slacks



# Making a network timing feasible

---

- ◆ **Naive approach:**



- ▲ Mark vertices with negative slacks
- ▲ Apply transformations to marked vertices

- ◆ **Redefined approach:**

- ▲ Transform multiple I/O delay constraints into single constraint by delay padding
- ▲ Apply algorithms for CP minimization
- ▲ Stop when constraints are satisfied

# Example

$$\bar{t} = [2332]^T$$

  

# Summary

---

- ◆ **Timing optimization is crucial for achieving competitive logic design**
- ◆ **Timing optimization problems are hard:**
  - ▲ **Detection of critical paths**
    - ▼ **Elimination of false paths**
  - ▲ **Network transformations**