

Logic synthesis: exercises

November 25, 2020

1 Two-level minimization

Let us consider the following incompletely specified function, where f represents the on-set and d the don't care set:

$$\begin{aligned}f &= \bar{a}\bar{b}c + bcd + \bar{a}b\bar{c}d + a\bar{b}c \\d &= \bar{a}\bar{b}\bar{c} + \bar{a}\bar{c}\bar{d} + ab\bar{c}d\end{aligned}$$

- Compute all prime implicants and identify the essential primes.
- Find a cover that minimizes the number of literals of the SOP.
- Find a cover that minimizes the number of variables in the support of the SOP.

2 Multi-level optimization

Let us consider the following Boolean network with two nodes:

$$\begin{aligned}x &= abd + bc + be + abg + ae \\y &= ade + cd + ce + ef + h\end{aligned}$$

- Calculate the kernels of both functions.
- Extract the best multi-cube common divisor.
- Create a new node with the divisor and substitute in the previous expressions.

3 Technology mapping

Consider a gate library that only has three gates: 2-input NAND, 2-input NOR and inverter. The area cost of the NAND and NOR gates is 2, whereas the inverter has cost 1. We want to do technology mapping using only 2-input NAND gates and inverters as base functions in the target graph. Answer the following questions:

- Draw the library patterns for the gates in the library using the base functions.
- Consider the following function:

$$f = a_1b_1 + a_2b_2 + a_3b_3 + a_4b_4.$$

Draw the most balanced target graph in terms of the base functions and find the most efficient mapping.

- Let us assume that every gate has delay=1 and that the arrival time of all signals is $t = 0$, except for b_4 whose arrival time is $t = 10$. Draw the target graph that minimizes delay and find the most efficient mapping.

4 Binary Decision Diagrams


Let us consider two Boolean vectors, (a_{n-1}, \dots, a_0) and (b_{n-1}, \dots, b_0) , representing the binary encoding of two natural numbers a and b . Let us consider the BDD of a Boolean function that is *true* when $a < b$ and *false* when $a \geq b$.

- What is the variable order that minimizes the BDD size?
- What is the variable order that maximizes the BDD size?

Justify the previous answers and give an asymptotic complexity (using $O()$) of the BDD size for each case. Draw the BDD of the function considering the best variable order.

5 Retiming

 Consider the sequential network shown in the figure, where the rectangles represent registers and the circles represent combinational gates with unit delay.



Answer the following questions:

- What is the minimum period required for the network with the configuration of registers shown in the figure?
- What is the minimum period P_{\min} achievable after retiming?
- is the minimum number of registers R_{\min} achievable after retiming?
- For all solutions with period equal to P_{\min} find one with the minimum number of registers.
- For all solutions with R_{\min} registers, find one with minimum period.

Draw a picture with the solutions obtained from the previous questions.