

Libraries and Mapping

Giovanni De Micheli
Integrated Systems Centre
EPF Lausanne



This presentation can be used for non-commercial purposes as long as this note and the copyright footers are not removed

© Giovanni De Micheli – All rights reserved

Module 1

◆ Objective

- ▲ Libraries. Problem formulation and analysis
- ▲ Algorithms for library binding based on structural methods

Library binding

- ◆ **Given an unbound logic network and a set of library cells**
 - ▲ **Transform into an interconnection of instances of library cells**
 - ▲ **Optimize delay**
 - ▼ (under area or power constraints)
 - ▲ **Optimize area**
 - ▼ Under delay and/or power constraints
 - ▲ **Optimize power**
 - ▼ Under delay and/or area constraints
- ◆ **Library binding is called also technology mapping**
 - ▲ **Redesigning circuits in different technologies**

Major approaches

◆ Rule-based systems

- ▲ Generic, handle all types of cells and situations
- ▲ Hard to obtain circuit with specific properties
- ▲ Data base:
 - ▼ Set of pattern pairs
 - ▼ Local search: detect pattern, implement its best realization








◆ Heuristic algorithms

- ▲ Typically restricted to single-output combinational cells
- ▲ Library described by cell functionality and parameters

◆ Most systems use a combination of both approaches:

- ▲ Rules are used for I/Os, high buffering requirements, ...

Example

       

Library binding: issues

◆ Matching:

- ▲ A cell matches a sub-network when their terminal behavior is the same
- ▲ Tautology problem
- ▲ *Input-variable* assignment problem

◆ Covering:

- ▲ A cover of an unbound network is a partition into sub-networks which can be replaced by library cells.
- ▲ Binate covering problem

Assumptions

- ◆ **Network granularity is fine**

- ▲ **Decomposition into base functions:**

- ▲ 2-input **AND, OR, NAND, NOR**


- ◆ **Trivial binding**

- ▲ **Use base cells to realize decomposed network**


- ▲ **There exists always a trivial binding:**

- ▼ **Base-cost solution...**


Example

 


(a)

 

(b)



 


(c)

 

(d)



Example

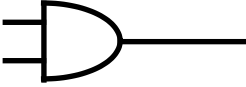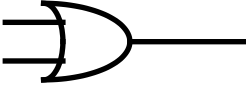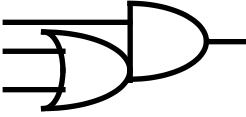Library	Cost
 AND2	4
 OR2	4
 OA21	5

$$x = b + c$$

$$y = ax$$

$$z = xd$$

  


$$m_1: \{v_1, \text{OR2}\}$$

$$m_2: \{v_2, \text{AND2}\}$$

$$m_3: \{v_3, \text{AND2}\}$$

$$m_4: \{v_1, v_2, \text{OA21}\}$$

$$m_5: \{v_1, v_3, \text{OA21}\}$$

 

Example

◆ Vertex covering:

▲ Covering $v_1 : (m_1 + m_4 + m_5)$

▲ Covering $v_2 : (m_2 + m_4)$

▲ Covering $v_3 : (m_3 + m_5)$

◆ Input compatibility:

▲ Match m_2 requires m_1


▼ $(m'_2 + m_1)$

▲ Match m_3 requires m_1

▼ $(m'_3 + m_1)$

◆ Overall binate covering clause

 ▲ $(m_1 + m_4 + m_5)(m_2 + m_4)(m_3 + m_5)(m'_2 + m_1)(m'_3 + m_1) = 1$



Heuristic approach to library binding

- ◆ Split problem into various stages:

- ▲ Decomposition

- ▼ Cast network and library in standard form
 - ▼ Decompose into base functions
 - ▼ Example, **NAND2** and **INV**

- ▲ Partitioning

- ▼ Break network into cones
 - ▼ Reduce to many **multi-input, single-output** networks


- ▲ Covering

- ▼ Cover each sub-network by library cells


- ◆ Most tools use this strategy

- ▲ Sometimes stages are merged


Decomposition

 

Partitioning

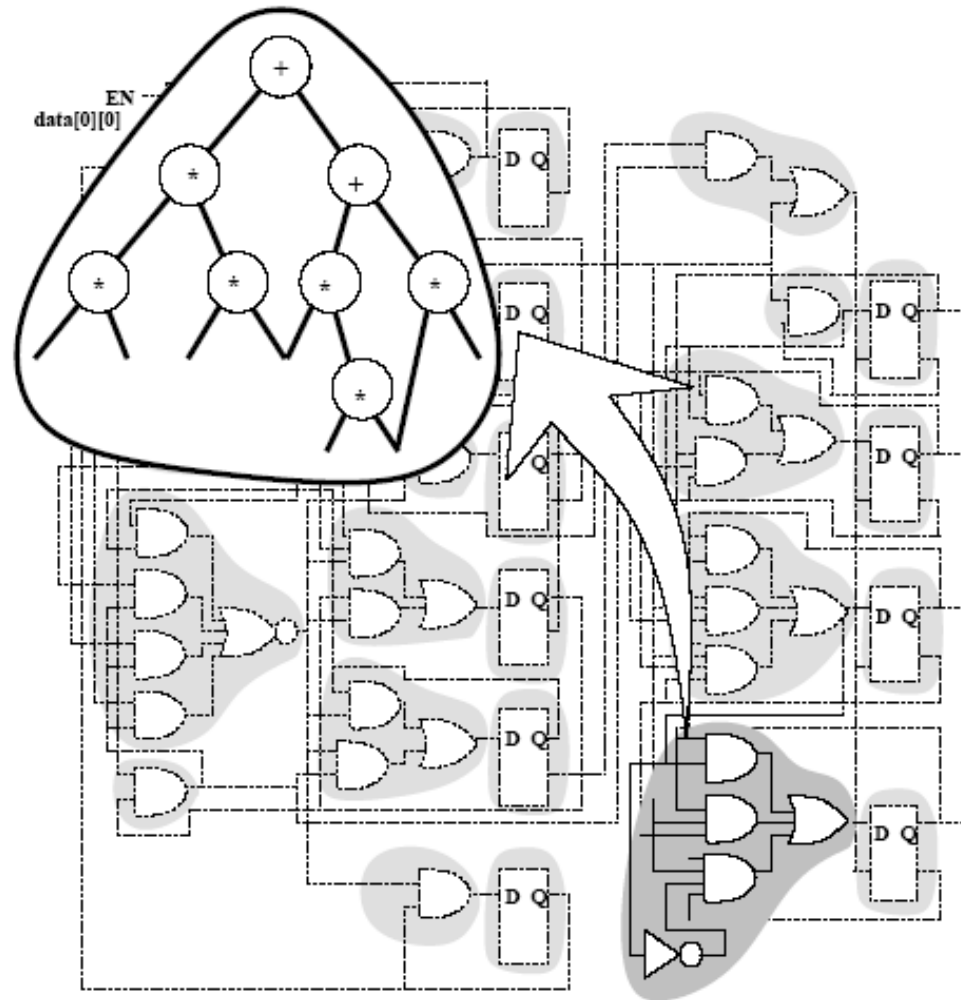

Covering

 

Heuristic algorithms

◆ Structural approach

▲ Model functions by patterns

▼ Example: tree, dags

▲ Rely on pattern matching techniques

◆ Boolean approach

▲ Use Boolean models

▲ Solve the tautology problem

▼ Use BDD technology

▲ More powerful

Example

- ◆ Boolean vs. structural matching

- ◆ $f = xy + x'y' + y'z$



- ◆ $g = xy + x'y' + xz$

- ◆ Function equality is a tautology

 - ▲ Boolean match

- ◆ Patterns may be different





 - ▲ Structural match may not exist

  

Structural matching and covering

- ◆ Expression patterns
 - ▲ Represented by dags
- ◆ Identify pattern dags in network
 - ▲ Sub-graph isomorphism
- ◆ Simplification:
 - ▲ Use tree patterns
- ◆ Typical problems with **EXORs** and **MAJ**ority functions

Example

    

Tree-based matching

◆ Network:

▲ Partitioned and decomposed

- ▼ NOR2 (or NAND2) + INV

- ▼ Generic base functions

 - ◆ Not much used

- ▼ Subject tree

◆ Library

- ▲ Represented by trees


- ▲ Possibly more than one tree per cell

◆ Pattern recognition

- ▲ Simple binary tree match

- ▲ Aho-Corasik automaton

Simple library

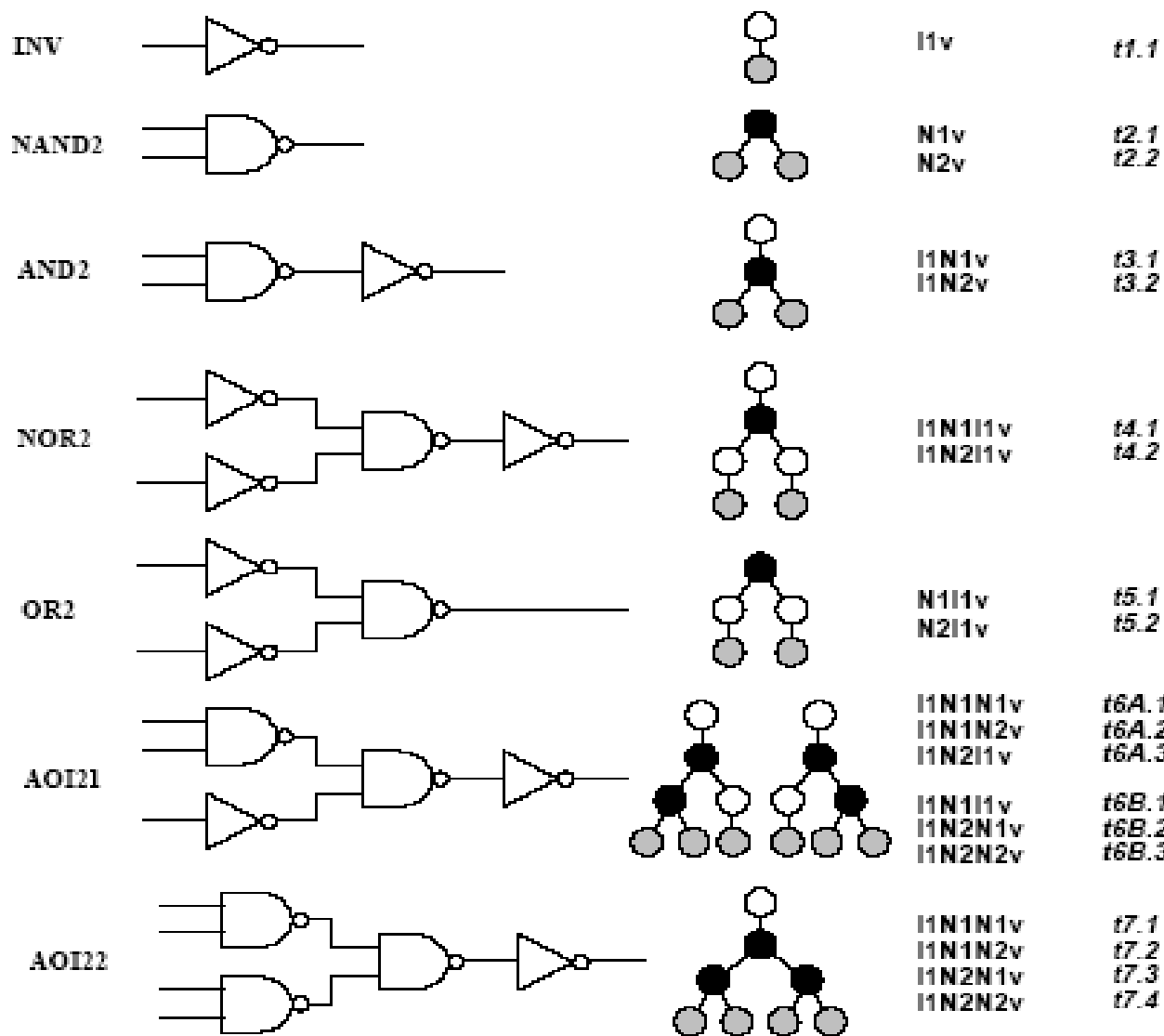


Tree covering

- ◆ **Dynamic programming**
 - ▲ Visit subject tree bottom up
- ◆ **At each vertex**
 - ▲ Attempt to match:
 - ▼ Locally rooted subtree to all library cell
 - ▼ Find best match and record
 - ▲ There is always a match when the base cells are in the library
- ◆ **Bottom-up search yields and optimum cover**
- ◆ **Caveat:**
 - ▲ Mapping into trees is a distortion for some cells
 - ▲ Overall optimality is weakened by the overall strategy of splitting into several stages

Example


SUBJECT TREE

 


PATTERN TREES




cost = 2
INV

 

cost = 3
NAND

 


cost = 4
AND

 

cost = 5
OR

Example: Lib

 

Match of s: t1
cost = 2






Match of t: t1
cost = 2+3 = 5

Match of t: t3
cost = 4

Match of r: t2
cost = 3+2+4 = 9

Match of r: t4
cost = 5+3 = 8


Match of u: t2
cost = 3

     

Different covering problems

- ◆ **Covering for minimum area:**
 - ▲ Each cell has a fixed area cost (label)
 - ▲ Area is additive:
 - ▼ Add area of match to cost of sub-trees
- ◆ **Covering for minimum delay:**
 - ▲ Delay is fanout independent
 - ▼ Delay computed with (max, +) rules
 - ▼ Add delay of match to highest cost of sub-trees
 - ▲ Delay is fanout dependent
 - ▼ Look-ahead scheme is required

Simple library

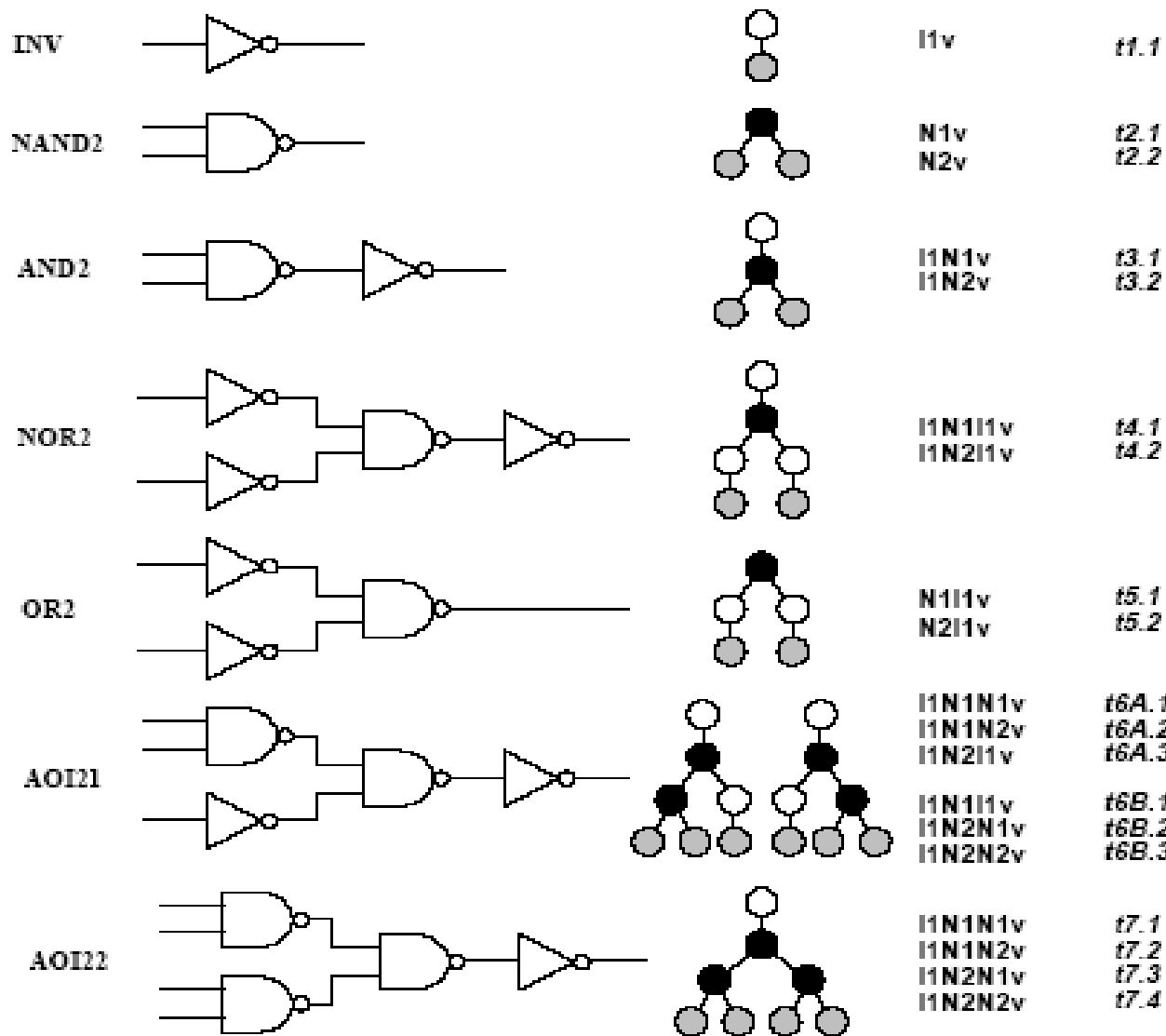



Example – minimum area cover

◆ Area cost: INV:2 NAND2:3 AND2: 4 AOI21: 6

Network	Subject graph	Vertex	Match	Gate	Cost
		x	t2	NAND2(b,c)	3
		y	t1	INV(a)	2
		z	t2	NAND2(x,d)	$3+3 = 6$
		w	t2	NAND2(y,z)	$3+6+ 2 = 11$
		o	t1	INV(w)	$2+11 = 13$
			t3	AND2(y,z)	$6 + 4 + 2 = 12$
			t6B	AOI21(x,d,a)	$6 + 3 = 9$

Example – minimum delay cover

- Fixed delays: **INV:2** **NAND2:4** **AND2: 5** **AOI21: 10**
- All inputs are stable at time 0, except for $t_d = 6$

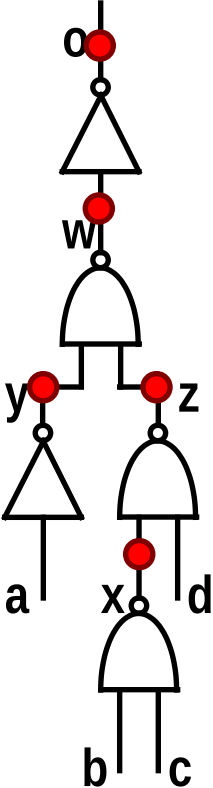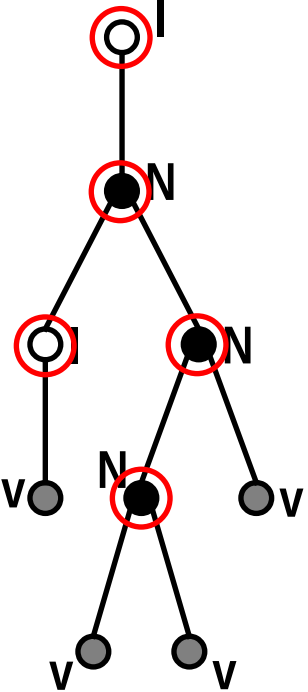Network	Subject graph	Vertex	Match	Gate	Cost
		x	t2	NAND2(b,c)	4
		y	t1	INV(a)	2
		z	t2	NAND2(x,d)	6+4 = 10
		w	t2	NAND2(y,z)	10 + 4 = 14
		o	t1	INV(w)	14 + 2 = 16
			t3	AND2(y,z)	10 + 5 = 15
			t6B	AOI21(x,d,a)	10 + 6 = 16

Minimum-delay cover for load-dependent delays

◆ Model

- ▲ Gate delay is $d = \alpha + \beta \text{ cap_load}$
- ▲ Capacitive load depends on the driven cells (fanout cone)
- ▲ There is a finite (possibly small) set of capacitive loads

◆ Algorithm

- ▲ Visit subject tree bottom up
- ▲ Compute an array of solutions for each possible load
- ▲ For each input to a matching cell, the best match for the corresponding load is selected

◆ Optimality

- ▲ Optimum solution when all possible loads are considered
- ▲ Heuristic: group loads into bins

Example – minimum delay cover



- ◆ Delays: **INV:1+load** **NAND2: 3+load** **AND2: 4+load** **AOI21: 9+load**
- ◆ All inputs are stable at time 0, except for $t_d = 6$
- ◆ All loads are 1 Same as before !

Network	Subject graph	Vertex	Match	Gate	Cost
		x	t2	NAND2(b,c)	4
		y	t1	INV(a)	2
		z	t2	NAND2(x,d)	6+4 = 10
		w	t2	NAND2(y,z)	10 + 4 = 14
		o	t1	INV(w)	14 + 2 = 16
			t3	AND2(y,z)	10 + 5 = 15
			t6B	AOI21(x,d,a)	10 + 6 = 16

Example – minimum delay cover

- ◆ Delays: **INV**: 1+load **NAND2**: 3+load **AND2**: 4+load **AOI21**: 9+load
- ◆ All inputs are stable at time 0, except for $t_d = 6$
- ◆ All loads are 1 (for cells seen so far)
- ◆ Add new cell **SINV** with delay $1 + \frac{1}{2} \text{load}$ and load **2**
- ◆ The sub-network drives a load of 5

Example – minimum delay cover

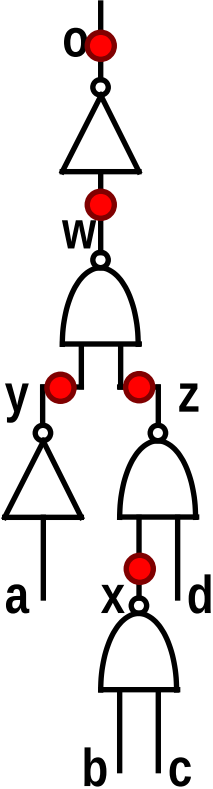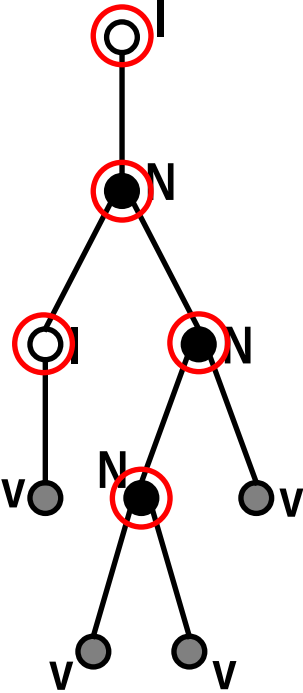Network	Subject graph	Vertex	Match	Gate	Cost		
					Load=1	Load=2	Load=5
		x	t2	NAND2(b,c)	4	5	8
		y	t1	INV(a)	2	3	6
		z	t2	NAND2(x,d)	10	11	14
		w	t2	NAND2(y,z)	14	15	18
		o	t1	INV(w)			20
			t3	AND2(y,z)			19
			t6B	AOI21(x,d,a) SINV(w)			20 18.5





Library binding and polarity assignment

- ◆ Search for lower cost solutions allowing signals to be generated with inverted polarity
 - ▲ More cells to choose from
- ◆ Polarities can be adjusted at register and/or I/O boundaries
- ◆ Within structural covering:
 - ▲ Polarity assignment is handled by a smart trick
- ◆ Within structural covering
 - ▲ Polarity assignment is built into the formulation

Structural covering and polarity assignment

- ◆ Assume subject network is decomposed into base functions such as **NAND2** and **INV**
- ◆ Pre-process subject network by adding inverter pairs between **NANDs**
- ◆ Provide I/Os with both polarity
- ◆ Add to library inverter-pair cell **2INV** to the library:
 - ▲ Cell corresponds to a connection and has **0** cost
 - ▲ Unnecessary **2INV** will be removed by the algorithm
- ◆ Apply bottom-up dynamic programming cover algorithm

Example

    

General issues with covering

- ◆ **Decomposition and covering yield solutions that are locally sub-optimal at multiple fanout points**
 - ▲ Covering in various logic cones is independent
 - ▲ High capacitive loads skews the solution
- ◆ **Approaches**
 - ▲ **Implicit decomposition methods**
 - ▼ Compute and map all possible decompositions of a network
 - ▲ **Cell *cloning* and buffering at cone vertices**
 - ▲ **Wavefront mapping**

Wavefront mapping

- ◆ A *wavefront* is a sub-network
 - ▲ Cutting all I/O paths
 - ▲ With width W
- ◆ When W is the circuit depth, then covering for load-dependent delays is optimum
- ◆ For reasonably smaller values of W , optimality is preserved
 - ▲ The wavefront can be dynamically decomposed
 - ▲ The wavefront can be mapped (with duplications) for delay or other objectives

Buffering

◆ Drive multiple sinks:

- ▲ Possibly with +/- polarities
- ▲ Possibly with different loads
- ▲ Possibly with different criticality

◆ Logic/electrical effort theory


- ▲ $\text{delay} = p + q \text{ gain}$
- ▲ $\text{gain} = \text{load}/C_{in}$ is a design parameter

◆ Issues:

- ▲ Determine minimal buffer tree delay
- ▲ Determine tree with minimal load
 - ▼ satisfying all timing constraint

◆ Solutions:

- ▲ Make electrical effort uniform in chains
 - ▼ Closed form solution
- ▲ Adapt to non-continuous cell sizes and tree structure
 - ▼ Gain based algorithm

 


Module 2

◆ Objectives

- ▲ Boolean covering
- ▲ Boolean matching
- ▲ Simultaneous optimization and binding
- ▲ Extensions to Boolean methods

Boolean covering

 - ◆ Decompose network into base functions
- ◆ Partition network into cones
- ◆ Apply bottom-up covering to each cone
 - ▲ When considering vertex v :
 - ▼ Construct clusters by local elimination
 - ▼ Limit the depth of the cluster by limiting the support of the function
 - ▼ Associate several functions with vertex v
 - ▼ Apply matching and record cost



$$\begin{aligned}f_{j,1} &= xy; \\f_{j,2} &= x(a + c); \\f_{j,3} &= (e + z)y; \\f_{j,4} &= (e + z)(a + c); \\f_{j,5} &= (e + c' + d)y; \\f_{j,6} &= (e + c' + d)(a + c); \end{aligned}$$

Boolean matching

P -equivalence

- ◆ **Cluster function $f(x)$**

- ▲ Sub-network behavior

- ◆ **Pattern function $g(y)$**

- ▲ Cell behavior

- ◆ **P -equivalence**

- ▲ Is there a permutation operator P , such that $f(x) = g(Px)$ is a tautology?

- ◆ **Approaches:**

- ▲ Tautology check over all input permutations

- ▲ Multi-rooted pattern ROBDD capturing all permutations

Input/output polarity assignment


- ◆ ***NPN*** classification of logic functions
- ◆ ***NPN-equivalence***
 - ▲ There exist a permutation operator ***P*** and complementation operators ***N_i*** and ***N_o***, such that $f(x) = N_o g (P N_i x)$ is a tautology
- ◆ **Variations:**
 - ▲ ***N-equivalence***
 - ▲ ***PN-equivalence***

Boolean matching

◆ Pin assignment problem:


▲ Map cluster variables x to pattern variables y

▲ Characteristic equation: $A(x,y) = 1$

 

◆ Pattern function under variable assignment:

▲ $g_A(x) = S_y (A(x,y) g(y))$

 

◆ Tautology problem

▲ $f(x) = g_A(x)$

▲ $\forall_x f(x) = S_y (A(x,y) g(y))$

Example

◆ Cluster terminals: x -- cell terminals: y

◆ Assign x_1 to y'_2 and x_2 to y_1

◆ Characteristic equation


$$\blacktriangle A(x_1, x_2, y_1, y_2) = (x_1 \oplus y_2)(x_2 \oplus y_1)$$

◆ AND pattern function

$$\blacktriangle g = y_1 y_2$$

◆ Pattern function under assignment
 
$$\blacktriangle S_{y_1 y_2} A g = S_{y_1 y_2} ((x_1 \oplus y_2)(x_2 \oplus y_1) y_1 y_2) = x_2 x'_1$$



Signatures and filters

- ◆ Capture some properties of Boolean functions
- ◆ If signatures do not match, there is no match
- ◆ Signatures are used as filters to reduce computation
- ◆ Signatures:
 - ▲ Unateness
 - ▲ Symmetries
 - ▲ Co-factor sizes
 - ▲ Spectra

Filters based on unateness and symmetries

- ◆ Any pin assignment must associate:
 - ▲ Unate variables in $f(x)$ with unate variables in $g(y)$
 - ▲ Binate variables in $f(x)$ with binate variables in $g(y)$
- ◆ Variables or group of variables:
 - ▲ That are interchangeable in $f(x)$ must be interchangeable in $g(y)$

Example

- ◆ Cluster function: $f = abc$

- ▲ Symmetries $\{ \{a,b,c\} \}$

- ▲ Unate

- ◆ Pattern functions

- ▲ $g_1 = a + b + c$

- ▼ Symmetries $\{ \{a,b,c\} \}$

- ▼ Unate

- ▲ $g_2 = ab + c$

- ▼ Symmetries $\{ \{a,b\}, \{c\} \}$

- ▼ Unate

- ▲ $g_3 = abc' + a'b'c$

- ▼ Symmetries $\{ \{a,b,c\} \}$

- ▼ Binate

Concurrent optimization and library binding


◆ Motivation

- ▲ Logic simplification is usually done prior to binding
- ▲ Logic simplification and substitution can be combined with binding

◆ Mechanism

- ▲ Binding induces some *don't care* conditions
- ▲ Exploit *don't cares* as degrees of freedom in matching

Example

 

Boolean matching with *don't care* conditions

◆ Given $f(x)$, $f_{DC}(x)$ and $g(y)$

▲ g matches f , if g is equivalent to h , where:



$$f \vee f'_{DC} \leq h \leq f + f_{DC}$$

◆ Matching condition:



$$\forall_x (f_{DC}(x) + f(x) \oplus S_y (A(x,y) g(y)))$$

  Example

- ◆ Assume v_x is bound to an $OR3(c',b,e)$
- ◆ Don't care set includes $x \oplus (c'+b+e)$
- ◆ Consider $f_j = x(a+c)$ with $CDC = x'c'$
- ◆ No simplification.
 - ▲ Mapping into AOI gate.
- ◆ Matching with DCs.
 - ▲ Map to a MUX gate.



Example

  

Extended matching

- ◆ **Motivation:**

- ▲ Search implicitly for best pin assignment
- ▲ Make a single test, determining matching and assignment

- ◆ **Technique:**

- ▲ Construct BDD model of cell and assignments

- ◆ **Visual intuition:**

- ▲ Imagine to place **MUX** function at cell inputs
- ▲ Each cell input can be routed to any cluster input (or voltage rail)
- ▲ Input polarity can be changed
- ▲ Cell and cluster may differ in size

- ◆ **Cell and multiplexers are described by a composite function $G(x,c)$**

- ▲ Pin assignment is determining **c**

- ◆ **Matching formula $M(c) = \forall_x [G(x,c) \oplus f(x)]$**


Example

◆ $g = y_1 + y_2 y_3'$

◆ $y_1(c,x) = (c_0 c_1 x_1 + c_0 c_1' x_2 + c_0' c_1 x_3) \oplus c_2$



◆ $G = y_1(c,x) + y_2(c,x) y_3(c,x)'$

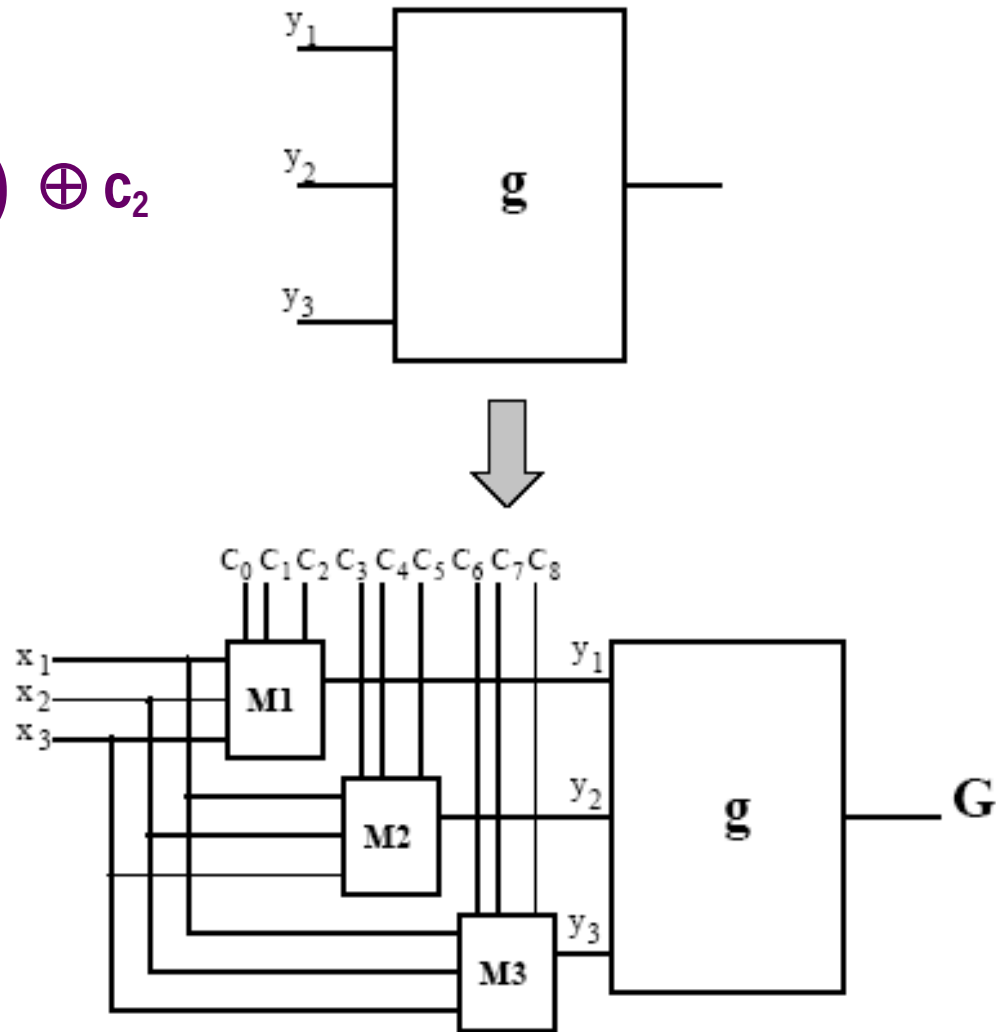

Extended matching modeling

- ◆ Model composite functions with ROBDDs
 - ▲ Assume n -input cluster and m -input cell
 - ▲ For each cell input:
 - ▼ $\lceil \log_2 n \rceil$ variables for pin permutation
 - ▼ One variable for input polarity
 - ▲ Total size of c : $m(\lceil \log_2 n \rceil + 1)$
- ◆ A match exists if there is at least one value of c satisfying
$$M(c) = \bigvee_x [G(x,c) \oplus f(x)]$$

Example



◆Cell: $g = x'y$

◆Cluster: $f = wz'$

◆ $G(a,b,c,d) = (c \oplus (za + wa'))'(d \oplus zb + wb')$

◆ $f \oplus G = (wz') \oplus (c \oplus (za + wa'))'(d \oplus zb + wb')$

◆ $M(c) = ab'c'd' + a'bcd$

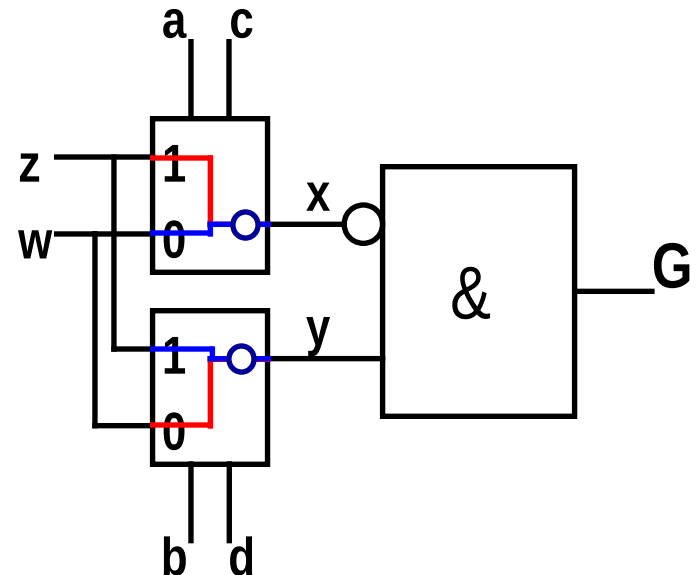 

Extended matching

- ◆ Extended matching captures implicitly all possible matches
- ◆ No extra burden when exploiting *don't care* sets
- ◆ $M(c) = \forall_x [G(x,c) \underline{\oplus} f(x) + f_{DC}(x)]$
- ◆ Efficient BDD representation
- ◆ Extensions:
 - ▲ Represent full library with one BDD structure
 - ▼ Visualize as MUX at output of all library cells
 - ▼ Composite function will indicated cell selection implicitly
 - ▲ Support multiple-output matching

Summary

- ◆ **Library binding is a key step in synthesis**
- ◆ **Most systems use some rules together with heuristic algorithms that concentrate on combinational logic**
 - ▲ **Best results are obtained with Boolean matching**
 - ▲ **Sometimes structural matching is used for speed**
- ◆ **Library binding is tightly linked to buffering and to physical design**